

2021/TDC(CBCS)/EVEN/SEM/ PHSDSE-602T/099

TDC (CBCS) Even Semester Exam., September—2021
6. What do you mean by interbase resistance? COUNTY COUNT
7. Fill in the blank; and all of the depletion layer of tunnel diode is very small bT206-32d2Hq: .oN asruo
(Physics of Devices and Communications). Second Devices and Communications Second Devices and Communications). Full Marks: 70 Pass Marks: 28 and communications Pull Marks: 28 and communications
Time: 3 hours The figures in the margin indicate full marks for the questions
11. Write the expression for repel factor for a full-wave rectifier.
nswer any <i>twenty</i> questions: 1×20=20
12. Draw the output voltage waveform of a learnest large large state. In an area large large state output voltage waveform of a learnest large large large large state. Take the contract large
13. Draw the waveform of an astable multivibrate.TET in FET.
3. Why MOSFET is also called IGFET?
4. Draw the characteristic curve of a UJT.
2J /95 (Turn Over.)

- 5. How many PN junction diode the UJT consists of?
- 6. What do you mean by interbase resistance?
- 7. Fill in the blank:

 The depletion layer of tunnel diode is very small because _____.
- 8. Why are tunnel diodes made up of germanium and silicon semiconductors?
- 9. Draw the block diagram of a power supply.
- 10. Write two limitations of an unregulated power supply.
- 11. Write the expression for repel factor for a full-wave rectifier.
- **12.** Draw the output voltage waveform of a rectified and filtered half-wave rectifier.
- **13.** Draw the waveform of an astable multivibrator.
- **14.** What is the function of commutating capacitors in a transistorized multivibrator?

y.

- 15. What is the full form of PLL?
- 16. What do you mean by voltage controlled oscillator?

(3)

- 17. What do you mean by photomasking?
- 18. Write two drawbacks of integrated circuits.
- 19. How many masks are required to complete an IC?
- **20.** How capacitors are made during the fabrication of integrated circuits?
- 21. Define optical lithography.
- 22. How integrated resistors are made in ICs?
- 23. What do you mean by the lattice of a crystal?
- 24. What is lift-off technique?
- 25. What is the full form of USB?
- 26. What is the full form of GPIB?
- 27. What do you mean by UART?

(Turn Over)

(Continued)

22J**/95**

(4)

(5)

	What are the elements of USB transfers?	1	37. What do you mean by demodulation? 84
29.	6. What do you mean by voltage convolled SOP sanirty and SU is not so that is the function of USB port and the substitute of the substitut	ı	49. Why noitalubom abutilqms in BRS eniled. 88. communication system?
	7. What do you mean by photomasking? Write any two standards of USB	-	39. Write one difference between PCM and PPM. 50. With a circuit diagram, explain briefly about AM desponding for more waveford more of the country and the country waveford more of the count
	g. Write two drawbacks of integrated chicago	1	amplitude modulation. SECTION—C
31.	How many masks are required to complete Write one advantage of using USB port over a	1	Answer any five ques Boundard 8×5=40
	COM port.	4	1=6×2 : snoitseup suit year and the basic differences between a
32.	0. How capacitors are made during the fabrication of integrated circuits? [abrication of integrated circuits?] Characteristics are made during the fabrication of integrated circuits?	2 2	41. Why FET is called a voltage controlled device? In and explain its price.
	1. Define optical lithography.	9	8=2+8 Define pinch-off and out-off voltages.
33.	.xsbni noitalubom eniped in lCs? How integrated resistors are made in lCs?	2 2	52. Distinguish between n-channel and ni noitalugar agailor fo noisearque att ni noitalugar agailor fo noisearque att ni noitalugar agail ni noitalugar agail ni noitalugar agail ni noitalugar agail ni ni noitalugar agail ni
34.	What is the full form of AM in electronic communication systems?	2	8=1- à full-wave rectifier. lannada que la juntion
	24. What is lift-off technique?	7	53. a ni ratili a gnisu fo vitesessan a filter in a rectifici. Show that the registration is independent of load resistance.
35.	Write one drawback of amplitude modulation over the frequency modulation.	0.73	45. Define positive and negative maskings. 54. A power supply of 20 V, 50 Hz a.c. source
	36. What is the full form of GPIB?	2 / 2	Ac willed a soul the and his Alectronic grade
36.	Write the equation of an an examplitude remodulated wave.		recuffication Given that $C = 1000 \mu F$.
	Sec. 17	4	47. Write various USB standards.
22J /	95 mf (Continued)	2	22J/95 (Turn Over)

(6)

- 48. Discuss briefly about GPIB signals and lines.
- 49. Why modulation is needed in electronic communication system?
- 50. With a circuit diagram, explain briefly about AM demodulator.

SECTION-C

Answer any five questions:

8×5=40

- 51. What are the basic differences between a

 JFET and a BJT? Draw the structure of an

 n-channel JFET and explain its principle of
 operation in brief.

 3+5=8
- **52.** Distinguish between *n*-channel and *p*-channel MOSFETs. Explain briefly the working of a *p*-channel MOSFET. 4+4=8
- **53.** Explain the action of *L*-section filter with a full-wave rectifier. Show that the repel factor is independent of load resistance.
- **54.** A power supply of 20 V, 50 Hz a.c. source provides 100 mA current. It uses a C-filter. Calculate the ripple factor of full-wave rectification. Given that $C = 1000 \,\mu\text{F}$.

10 11

8

8

(Continued)

(7)

8

8

8

8

- **55.** Describe the various steps used during an IC fabrication.
- 56. Distinguish between the process of optical lithography and electron lithography used during IC fabrication.
- **57.** What do you mean by handshaking? How GPIB is implemented on a personal computer? 3+5=8
- 58. What are the objectives behind the development of USB transfers? Explain its various standards used in digital electronic devices.

 3+5=8
- **59.** With a neat block diagram, describe the various stages of electronic communication system.
- **60.** Obtain the equation of an amplitude modulated wave with a clear explanation of its various terms.

* * *

2021/TDC(CBCS)/EVEN/SEM/ PHSDSE-602T/099

22J-50/95

22J**/95**