



**2022/TDC/ODD/SEM/
PHSHCC-303T/152**

TDC (CBCS) Odd Semester Exam., 2022

PHYSICS

(Honours)

(3rd Semester)

Course No. : PSHHCC-303T

(Digital Systems and Applications)

Full Marks : 50

Pass Marks : 20

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

UNIT—I

1. Answer any two of the following : 2×2=4

- (a) How is phase difference measured using CRO? Explain.
- (b) Explain active and passive components giving examples of each of them.
- (c) Convert 13.24 into its binary equivalent.



(2)

2. Answer any *one* of the following : 6

- (a) With the help of a structured block diagram, explain the working of its various units of a CRO. 2+4=6
- (b) Realize the circuit diagram of a two-input AND gate using discrete components and explain its working using its truth table.

UNIT—II

3. Answer any *two* of the following : 2×2=4

- (a) State and verify De Morgan's theorems.
- (b) What do you mean by minterms and maxterms?
- (c) Using Boolean algebra, simplify the following expression :

$$Y = (A \cdot B) \cdot (A + C)$$

4. Answer any *one* of the following : 6

- (a) With the help of an example, explain the sum of products method to convert a truth table to an equivalent Boolean expression. Draw the corresponding logic circuit. 4+2=6

(3)

- (b) What is the use of a multiplexer in digital communications? Using a block diagram, explain the working of a 4-to-1 multiplexer. 2+4=6

UNIT—III

5. Answer any *two* of the following : 2×2=4

- (a) Subtract 10100 from 11011 by 2's complement method.
- (b) What is a half-adder? With the help of its truth table, draw its logic circuit.
- (c) Explain the purposes of preset and clear functions in flip-flops.

6. Answer any *one* of the following : 6

- (a) Draw the block diagram of a J-K flip-flop and describe its working. What are race-around conditions in J-K flip-flop? 4+2=6
- (b) What is a subtractor? Explain the working of a full subtractor in detail with necessary truth table and logic diagram. 1+5=6



((4))

UNIT—IV

7. Answer any *two* of the following : $2 \times 2 = 4$

- (a) Explain a 4-bit serial-in parallel-out shift register.
- (b) Write a brief note on decade counters.
- (c) Briefly explain the terms 'RAM' and 'ROM'.

8. Answer any *one* of the following : 6

- (a) Write notes on the following : $3 \times 2 = 6$
 - (i) Asynchronous counter
 - (ii) Ring counter
- (b) Draw the internal organization of a digital computer and explain briefly the functions of its various units.

UNIT—V

9. Answer any *two* of the following : $2 \times 2 = 4$

- (a) Draw the block diagram of an IC555 showing simplified view of internal structures.

J23/201

(Continued)

(5)

(b) Draw the internal organizations of an 8085 microprocessor.

(c) Describe the functions of ALU used in microprocessors.

10. Answer any *one* of the following : 6

- (a) (i) What do you mean by 'bus' in digital microprocessors?
(ii) Describe the timing and control circuitry in microprocessors. $2+4=6$
- (b) With a proper circuit diagram, explain the working of an astable multivibrator using IC555. Obtain the formula for frequency of its oscillation. $4+2=6$

J23—350/201

2022/TDC/ODD/SEM/
PHSHCC-303T/152