



011
(M)

**2021/TDC/CBCS/ODD/
PHSHCC-303T/152**

**TDC (CBCS) Odd Semester Exam., 2021
held in March, 2022**

PHYSICS

(3rd Semester)

Course No. : PSHHCC-303T

(Digital Systems and Applications)

Full Marks : 50

Pass Marks : 20

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

SECTION—A

Answer any *ten* of the following questions :

2×10=20

1. Obtain the expression for deflection sensitivity of a CRO.
2. Give two examples each of linear and digital ICs.
3. Convert 4DF hexadecimal number to octal number.

(Turn Over)



(2)

4. What do you mean by minterms and maxterms?
5. Draw the block logic diagram of the following Boolean equation :
$$Y = AC + B\bar{C}$$
6. Write briefly about decoders.
7. Discuss how 2's complement method is used in representing a negative number.
8. What do you mean by race-around conditions in a *J-K* flip-flop?
9. Briefly describe the working of a 2-bit binary adder.
10. What is the function of shift registers in digital computers?
11. Describe briefly how data is stored in digital computers.
12. Write a brief note on ring counters.
13. Draw the block diagram of the organization of an 8085 microprocessor.

22J/690

(Continued)

(3)

14. Why is stack memory used in microprocessors?
15. Write MOV and MVI instructions used in 8085 microprocessor.

SECTION—B

Answer any five of the following questions : 6×5=30

16. Using labelled diagram, realize two-input OR and AND gates using diodes and hence explain their working. 3+3=6
17. (a) Explain active and passive components used in electronics with examples. 2
(b) Explain how phase difference between two sinusoidal signals is measured by using a CRO. 4
18. (a) Verify the following Boolean laws : 2
(i) $A \cdot \bar{A} = 0$
(ii) $A + \bar{A} = 1$
(b) State and prove De Morgan's laws. 4
19. (a) Simplify the following expression : 1
$$\overline{AB + \bar{A}} + AB$$

(b) What is a multiplexer? Explain the working of a 4-bit multiplexer. 5

22J/690

(Turn Over)



20. (a) What is the function of *D* flip-flop in digital electronics? 2
- (b) Develop the truth table for a half-adder and then draw its logic circuit diagram along with its Boolean expressions. 4
21. Explain the working of a *J-K* flip-flop with proper logic diagram. 6
22. Describe in detail about parallel-in parallel-out shift register used in digital computers. 6
23. With proper diagram, describe various functional units of a digital computer. 6
24. (a) Write an example of instruction code each for 1-byte and 2-byte instructions. 2
- (b) With proper diagram, describe the internal organization of an 8085 micro-processor. 4
25. Explain the pin-out configurations of a 555 timer IC. Explain its working as a monostable multivibrator of a given duration.

2+4=6
